

Electricity with the Modular System


Basic Electric Circuits
Electrical resistance

Relationship between
resistance and length
of a wire

Objective of the experiment

To investigate the relationship between resistance and length of a wire.

Setup

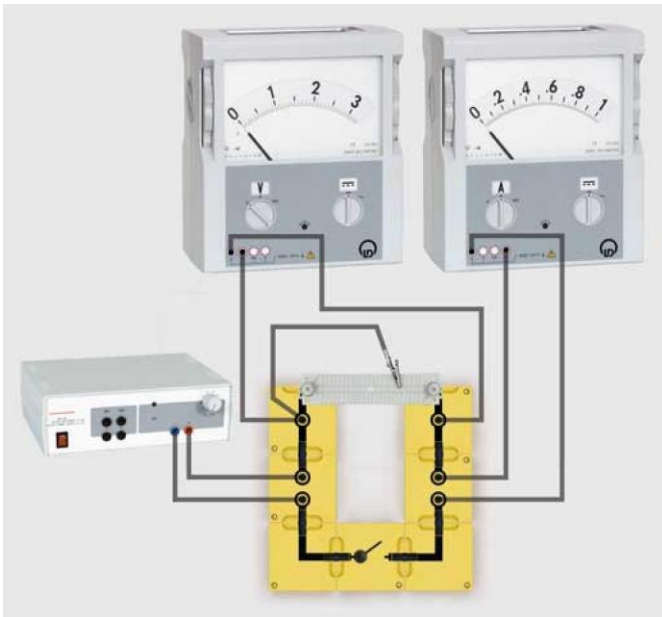

Apparatus

1	567 18	Wire wrapping plate
1	550 46	Chrome-nickel wire, $d = 0,25$ mm
2	539 060	Adapter plug, BST
1	539 025	Toggle switch, BST
2	539 002	Connector blocks BST, straight, 1 socket
2	539 003	Connector blocks BST, straight, 2 sockets
2	539 004	Connector blocks BST, 90° angle
6	539 000	Bridging plug, BST
2	531 906	Demo multimeter, passive
1	521 49	Power supply, 12 V DC, 230 V
6	500 644	Safety connection lead, 100 cm
1	500 411	Connection lead, 25 cm
1	from 501 861	Croc-clip
1	301 300	Demonstration experiment frame
1	301 301	Adhesive magnetic board

Carrying out the experiment

- Wind the chrome-nickel wire around the wire wrapping plate (25 turns) and clamp the ends of the wire used for contacting under the clamping screws.


Note: The wire length L per turn is about 8 cm.

- Set up the circuit and initially tap 6 turns of the wire wrapping plate with the crocodile clip.
- Close the switch and adjust the power supply to a voltage of approx. 3 V across the wire wrapping plate.
- Read the current and voltage from the multimeter and enter them into the table.
- Repeat the measurement with 12, 18 and 24 turns.
- Calculate the resistances R from voltages U and currents I .

Measuring example

Number of turns	L / cm	U / V	I / A	R / Ω
6	48	3	0.330	9
12	96	3	0.160	19
18	144	3	0.105	29
24	192	3	0.075	43

Evaluation

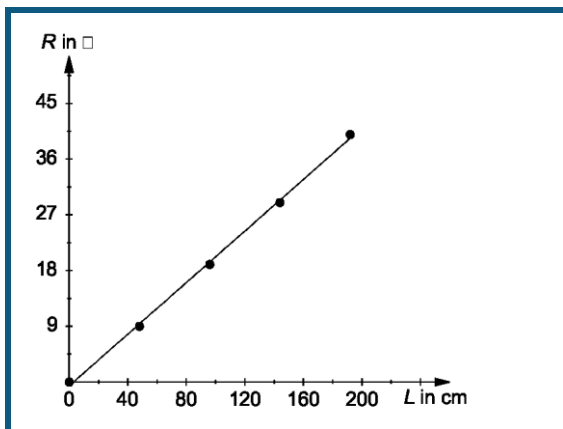

The resistance R of a wire increases proportionally to the length L of the wire: $R \sim L$.