

## Basic Electric Circuits

### Electric Resistance

Correlation between resistance and the cross-sectional area of a wire  
Set-up with the apparatus for resistance measurements

### Objects of the experiment

1. Investigating the correlation between resistance and cross-sectional area of a wire.

### Set-up



### Apparatus

1 Apparatus for resistance measurements .....	550 57
2 Demo-Multimeter, passive .....	531 906
1 Power supply, 12 V, DC, 230 V .....	521 49
5 Connecting leads, 100 cm .....	500 444
2 Stand base, V-shape .....	300 02
2 Stand rods, 250 mm .....	300 41
2 Leybold multiclamp .....	301 01
2 Metal plate .....	from 686 50 ET5


### Carrying out the experiment

- Connect the constantan-wire ( $d = 0,5 \text{ mm}$ ).
- Set a voltage of  $0,5 \text{ V}$  on the power supply.
- Read current and voltage and write it into the table.
- Repeat the measurement with Constantan-wires of identical length but diameters of  $d = 0,7 \text{ mm}$  and  $d = 1,0 \text{ mm}$ .
- Calculate the cross-sectional area  $A$  of the wires with diameter  $d$  ( $A = \pi r^2$ ).
- Calculate the resistances ( $R = \frac{U}{I}$ ) of the wires using voltages  $U$  and currents  $I$ .

### Measuring example

Voltage $U$ in V	0,5	0,5	0,5
Current $I$ in A	0,18	0,38	0,75
Resistance $R$ in $\Omega$	2,77	1,31	0,66
Diameter $d$ in mm	0,50	0,70	1,0
Cross-sectional area $A$ in $\text{mm}^2$	0,2	0,38	0,78
$\frac{1}{A}$ in $\frac{1}{\text{mm}^2}$	5,0	2,63	1,27

### Evaluation

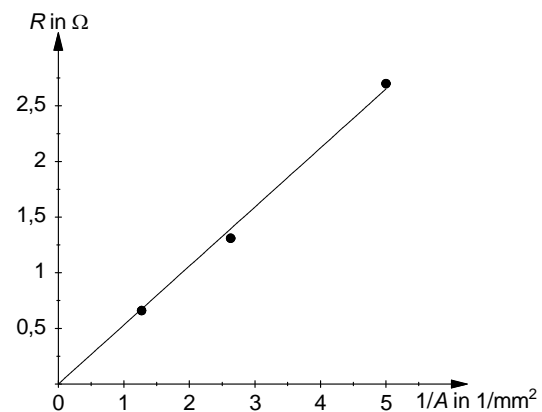

The resistance  $R$  of a wire increases inverse proportionally with its cross-sectional area  $A$ :  $R \sim \frac{1}{A}$ .