

# Electricity with the Modular System

Basic Electric Circuits  
Electrical resistance

Resistance characteristics  
of an incandescent lamp

## Objective of the experiment

1. To investigate the relationship between current and voltage in an incandescent lamp.
2. To determine the resistance characteristics of an incandescent lamp.

## Setup



## Apparatus

1	539 024	Lamp socket, E10, BST
1	505 15	Incandescent lamp 6 V / 0.05 A, E10
1	539 025	Toggle switch, BST
2	539 003	Connector blocks BST, straight, 2 sockets
2	539 004	Connector blocks BST, 90° angle
2	539 005	Connector blocks BST, 90° angle with socket
8	539 000	Bridging plug, BST
2	531 906	Demo multimeter, passive
1	521 49	Power supply, 12 V DC, 230 V
6	500 644	Safety connection lead, 100 cm
1	301 300	Demonstration experiment frame
1	301 301	Adhesive magnetic board


### Carrying out the experiment

- Set up the circuit.
- Switch on the power supply and gradually increase the voltage  $U$  between 0.4 V and 6 V. Read the current  $I$  in each case.
- Calculate the resistance of the incandescent lamp and enter it into the table.

### Measuring example

Voltage $U / V$	Current $I / A$	Resistance $R / \Omega$
0.4	0.011	36
0.6	0.013	46
0.8	0.016	50
1	0.018	55
2	0.027	74
3	0.034	88
4	0.040	100
5	0.045	111
6	0.050	120

### Evaluation

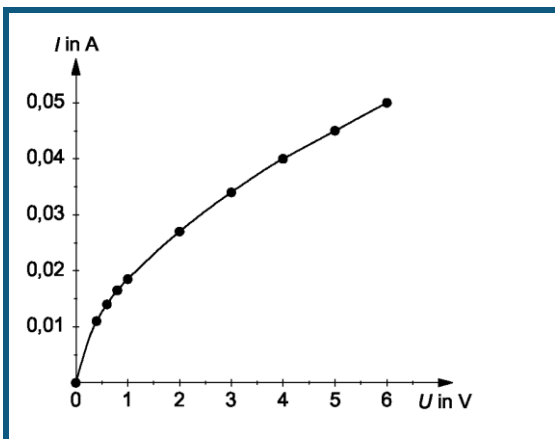

With an incandescent lamp, Ohm's Law does not apply because the current  $I$  doesn't change proportionally to the voltage  $U$ .

This is due to the temperature increase of the filament with the increasing current  $I$ .

The temperature increase leads to violent vibrations of the metal ions in the filament lattice. As a result, the movement of electrons (current) is strongly hindered. The resistance  $R$  of the filament increases.

Note:

In an incandescent lamp, we can distinguish between the cold resistance  $R_0$  and the operating resistance  $R_B$  (glowing filament). The following holds true:  $R_B \gg R_0$