

Electricity with the Modular System


Electromagnetism and Induction
Transformers

Voltage transformation

Objective of the experiment

To investigate the relationship between voltage U and the number of turns N in the primary and secondary circuits of an unloaded transformer.

Setup

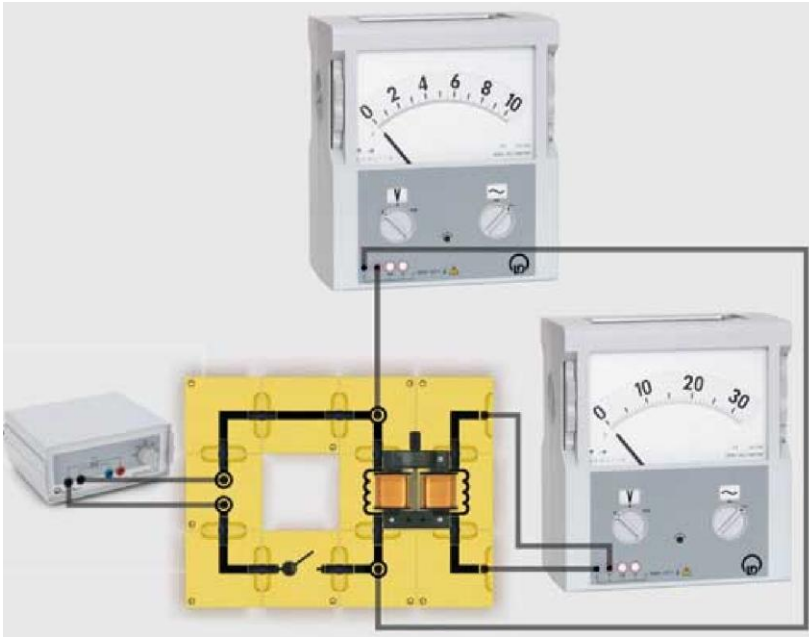

Apparatus

2	539 052	Coil holder, BST
1	590 83	Coil, STE, 500 turns
1	590 84	Coil, STE, 1000 turns
1	593 21	Transformer core, demountable
1	539 025	Toggle switch, BST
1	539 001	Connector block BST, straight
1	539 003	Connector block BST, straight, 2 sockets
4	539 004	Connector blocks BST, 90° angle
2	539 005	Connector block, BST, 90° angle, 1 socket
10	539 000	Bridging plug, BST
2	531 906	Demo multimeter, passive
1	521 230	Power supply, 3 V - 12 V, AC, 230 V
6	500 644	Safety connection lead, 100 cm
1	301 300	Demonstration experiment frame
1	301 301	Adhesive magnetic board

Carrying out the experiment

- Set up the circuit. To do this, first insert the coil with 500 turns (N_1) in the primary circuit and the coil with 1000 turns (N_2) in the secondary circuit.
- Adjust successively voltages of 3 V, 6 V and 9 V at the power supply.
- Read the voltages U_1 and U_2 from the demo multimeter in each case.
- Calculate quotients $\frac{U_1}{U_2}$ and enter them into the table.
- Now insert the coil with 1000 turns (N_1) in the primary circuit and the coil with 500 turns (N_2) in the secondary circuit and repeat the experiment.

Measuring example

$$\frac{N_1}{N_2} = \frac{500}{1000} = 0.5$$

Voltage step	Voltage U_1 / V	Voltage U_2 / V	$\frac{U_1}{U_2}$
3 V	2.8	5.2	0.53
6 V	6.0	11.0	0.54
9 V	9.0	17.5	0.51

$$\frac{N_1}{N_2} = \frac{1000}{500} = 2$$

Voltage step	Voltage U_1 / V	Voltage U_2 / V	$\frac{U_1}{U_2}$
3 V	2.8	1.2	2.3
6 V	6.0	2.6	2.3
9 V	9.0	4.1	2.2

Evaluation

In an unloaded transformer, the numbers of turns $\frac{N_1}{N_2}$ relate to each other as the voltages do.

$$\frac{N_1}{N_2} = \frac{U_1}{U_2}$$