

## Electronics with the Modular System

Basic Electronic Circuits  
Solar cells

## Short-circuit current of a solar cell

### Objective of the experiment

To measure the short-circuit current  $I_0$  of a solar cell as a function of the solar cell area  $A$ .

### Setup



### Apparatus

1	539 042	Solar cell, BST
2	539 004	Connector blocks BST, 90° angle
2	539 000	Bridging plug, BST
1	531 906	Demo multimeter, passive
2	500 644	Safety connection lead, 100 cm
1	301 300	Demonstration experiment frame
1	301 301	Adhesive magnetic board
additionally required		
1	500 644	Strip of cardboard approx. 5 cm x 10 cm

### Carrying out the experiment

Note

This experiment can be performed during normal daylight. Direct solar radiation is not necessary.


- Set up the circuit.
- Initially, cover the solar cell with a strip of cardboard.
- Pulling away the strip of cardboard, enlarge the solar cell area  $A$  by  $\frac{1}{4}$  intervals.
- Read the current  $I_0$  from the demo multimeter for each solar cell area  $A$ .

### Measuring example

Solar cell area $A$	Current $I_0$ / mA
$0 \cdot A_0$	0
$1/4 \cdot A_0$	18
$1/2 \cdot A_0$	35
$3/4 \cdot A_0$	48
$1 \cdot A_0$	64
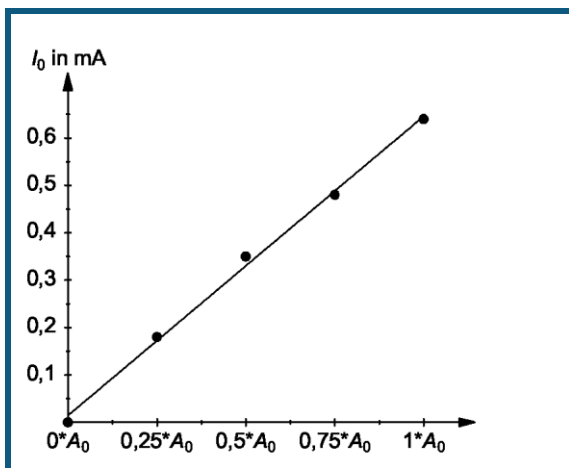
### Evaluation

An illuminated solar cell's measured current is known as its short-circuit current  $I_0$ .



The short-circuit current  $I_0$  is proportional to the area  $A$  of the solar cell:

$$I_0 \sim A.$$