

Electronics with the Modular System


Basic Electronic Circuits
Transistor Applications

Temperature-controlled transistor

Objective of the experiment

To demonstrate the working principle of a temperature-controlled transistor.

Setup

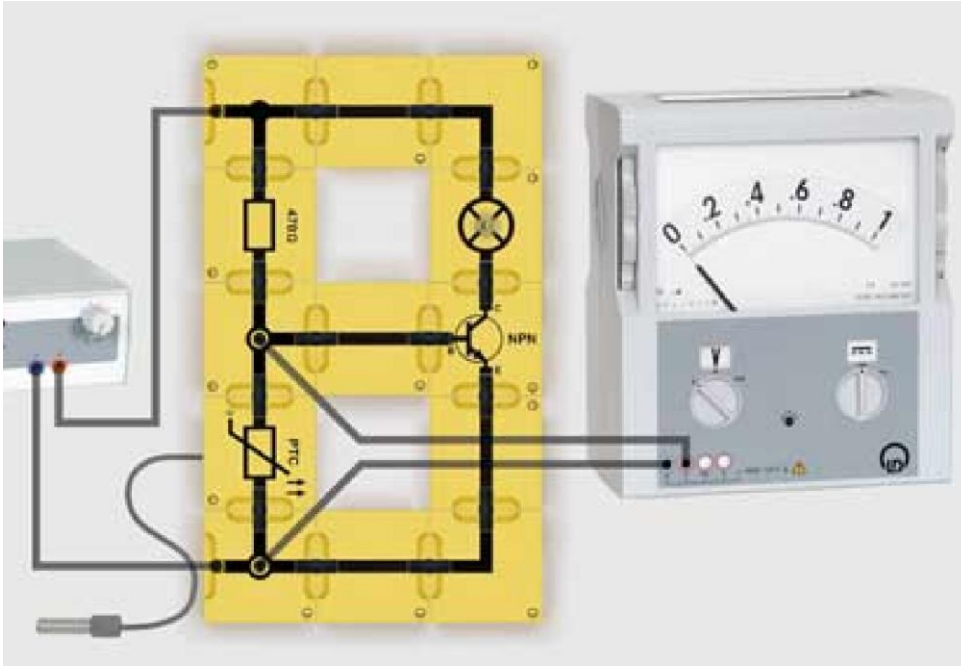

Apparatus

1	539 043	Transistor NPN, BD 137, BST	
1	539 022	PTC probe 30 Ω , BST	
1	539 010	Resistor 470 Ω , BST	
1	539 024	Lamp socket E10, BST	
1	from	505 15	Incandescent lamp, 6 V, 0.05 A, E10
4	539 001	Connector blocks BST, straight	
2	539 004	Connector blocks BST, 90° angle	
1	539 006	Connector block BST, T branch	
2	539 007	Connector blocks BST, T branch with socket	
14	539 000	Bridging plug, BST	
1	531 906	Demo multimeter, passive	
1	521 49	Power supply, 12 V DC, 230 V	
4	500 644	Safety connection lead, 100 cm	
1	301 300	Demonstration experiment frame	
1	301 301	Adhesive magnetic board	
additionally required			
1		Lighter	

Carrying out the experiment

- Adjust a voltage of approx. 6 V at the power supply.
- Observe the incandescent lamp at room temperature and read the voltage U_{BE} on the demo multimeter.
- Heat the PTC probe with a lighter.
- Observe the incandescent lamp again and read the voltage U_{BE} on the demo multimeter.

Observation and measuring example

PTC	U_{BE} / V	Lamp lit up
At room temperature	0.4	no
After heating with lighter	>0.7	yes

Evaluation

The resistance R of a PTC increases when heated (see Experiment D 4.1.1.1.b Temperature-dependent resistors).

The base-emitter voltage U_{BE} depends on the resistance R of the PTC. For low resistances R , the base-emitter voltage U_{BE} is below the threshold voltage $U_S = 0.6 V$. No collector current I_C flows. The lamp doesn't light up.

For very high resistances R the base-emitter voltage U_{BE} is above the threshold voltage U_S . A collector current I_C flows. The lamp lights up.

Based on the principle of the investigated circuit, a temperature-monitoring device can be built (e.g. for fire-prone rooms).

If the temperature exceeds the threshold value, an alarm system is activated.