

## The field-effect transistor as a switch

### Experiment Objectives

- Determination of the switch-on resistance.
- Measurement of the switch-off damping in the application as low-frequency circuit.

### Basic Information

As a field-effect, an electric field's action is denoted on electric load carriers. This effect is used with so-called field-effect transistors (FET). Unlike bipolar transistors, these use only one type of load carrier, which is why they are also designated as unipolar transistors. The field-effect transistors' advantage is in their ability to operate or to control current with no load.

Unlike bipolar NPN or PNP transistors, the field-effect transistor needs no control current, only a control voltage. The control electrode G (gate) works like a capacitor with an electric field that cancels the load carrier from the line channel between the source S and the drain D or enhances it. The gate input (gate-source path) is therefore very highly resistive.

So the field-effect transistor functions as a semiconductor resistor, for which the voltage applied to the gate G changes the conductivity or the resistance.

This experiment will first of all determine the source-drain path's forward resistance  $R_{SD}$  in the static case, where the gate and the drain are on the potential, i.e. the gate has a voltage  $U_G = 0$  V. In this situation the field-effect transistor connects through. For this reason, this resistance is designated as a switch-on resistance.

In the second part of the experiment, a low-frequency alternating voltage is applied as the input signal, and the output signal's dependence on the gate voltage  $U_{GS}$  is investigated. This signal is not completely disconnected, but only greatly damped. For the shut-off damping, we have:

$$d = 10 \cdot \log \left( \frac{U_E}{U_A} \right)^2 \quad (1)$$

### Apparatus

1 Plug-in board DIN A4 .....	576 74
1 Set of 10 bridging plugs .....	501 48
1 STE Transistor BF 244 (FET).....	578 77
1 STE Resistor 10 k $\Omega$ , 0.5 W .....	577 56
1 STE Resistor 47 k $\Omega$ , 0.5 W .....	577 64
1 STE Potentiometer 1 k $\Omega$ , 1 W .....	577 92
1 Function generator S 12.....	522 621
1 DC power supply 0...+/- 15 V .....	521 45
1 Multimeter LDanalog 20 .....	531 120
1 Two-channel oscilloscope 303 .....	575 211
2 Screened cables BNC/4 mm.....	575 24
2 Pairs of cables, 50 cm, red and blue .....	501 45
1 Pair of cables, 50 cm, black .....	501 451

### Setup

#### Procedure

##### a) Determination of the switch-on resistance

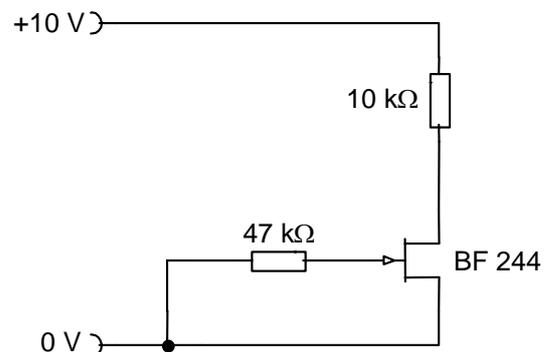


Illustration 1

- Experiment setup according to Illustration 1.
- Turn on the operating voltage and set it to 10 V.
- Measure the voltages at the resistor  $R_V (= 10\text{k}\Omega)$ ,  $U_{DS}$  and  $U_{GS}$ .

**b) Investigation of the gate voltage's influence**

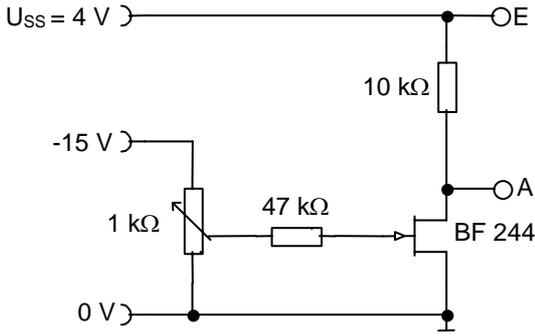


Illustration 2

- Circuit according to Illustration 2.
- Connect the oscilloscope to measure the input signal at E and the output signal at A.
- Connect the multimeter to measure the gate voltage  $U_{GS}$ .
- Turn on the operating voltage and set it to 15 V. Pay attention to the polarity in doing so.
- Supply a sinusoidal signal where  $U_S = 2\text{ V}$  and  $f = 1\text{ kHz}$ .
- Set the gate voltage  $U_{GS} = -10\text{ V}$  with the potentiometer. Observe the curves of the input voltage and output voltage with the oscilloscope.
- Reduce the gate voltage  $U_{GS}$  until the output curve begins to warp in the negative. Measure  $U_{GS}$ .
- Reduce the gate voltage  $U_{GS}$  more until the output curve begins to diminish in the positive. Measure  $U_{GS}$ .
- Reduce the gate voltage  $U_{GS}$  to 0 V. Measure  $U_{E,SS}$  and  $U_{A,SS}$  and calculate the switch-off damping according to (1).

**Measurement Examples**

**a) Determination of the switch-on resistance**

$U_{GS} = 0\text{ V}$


$U_{R_V}$	$U_{D_S}$
9.8 V	0.24 V

From  $I = \frac{U_{R_V}}{R} = \frac{9.8\text{ V}}{10\text{ k}\Omega} = 0.98\text{ mA}$  we get

$R_{SD} = R_{On} = \frac{U}{I} = \frac{0.24\text{ V}}{0.98\text{ mA}} = 245\ \Omega$

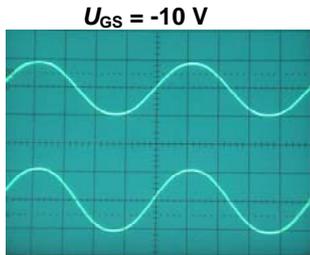
**b) Investigation of the gate voltage's influence**

Note: In each of the oscilloscope images, the input voltage is represented on top and the output voltage on the bottom.




Y I: 2 V/div DC  
Y II: 2 V/div DC  
Sweep: 0.2 msec/div

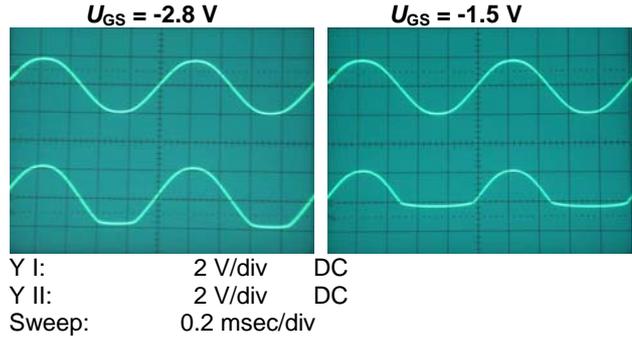- For a gate voltage  $U_{GS} = -10\text{ V}$  ( $R_{SD} \gg R_V$ ), an alternating voltage goes through undistorted:




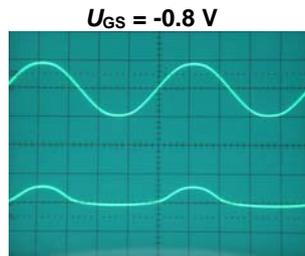- If the gate voltage is in the range  $-3\text{ V} < U_{GS} < -1.4\text{ V}$ , then the negative half-wave is damped. The positive half-wave goes through undistorted.



Y I: 2 V/div DC  
Y II: 2 V/div DC  
Sweep: 0.2 msec/div

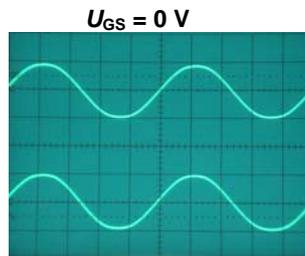- From a gate voltage of  $U_{GS} < -1.4\text{ V}$  a positive signal is also damped.



Y I: 2 V/div DC  
Y II: 50 mV/div DC  
Sweep: 0.2 msec/div

- For a gate voltage  $U_{GS} = 0\text{ V}$  ( $R_{SD} \ll R_V$ ), the alternating voltage goes through undistorted again, but it is severely damped or shifted. (The bottom curve's scale changes!):

**Attenuation calculation**

- The input signal  $U_{E,SS} = 4\text{ V}$  has declined to  $U_{A,SS} = 88\text{ mV}$ , so:

$\frac{U_A}{U_E} = \frac{0.088\text{ V}}{4\text{ V}} = 0.022$ ,

i.e. the input signal is attenuated by 97.8 % to 2.2%. That in turn corresponds to the ratio of the switch-on resistance  $R_{On}$  to the multiplier  $R_V$ :

$\frac{R_{On}}{R_V} = \frac{245\ \Omega}{10\text{ k}\Omega} = 0.0245$ .

- From (1), we have for the shut-off damping:

$d = 10 \cdot \log \left( \frac{4\text{ V}}{0.088\text{ V}} \right)^2 \approx 33\text{ dB}$