

## Basic Electric Circuits

## Electric Resistance

Correlation between the resistance and the material of a wire

Set-up with the apparatus for resistance measurements

## Objects of the experiment

1. Investigating the dependence of the resistance of a wire from its material.

## Set-up



## Evaluation

The resistance of a wire depends on its material.

Remark:

The material of an electrical conductor is characterized by a matter-specific quantity. That quantity is called specific electrical resistance:

$$\text{Symbol: } \rho \quad \text{Unit: } \frac{\Omega \cdot \text{mm}^2}{\text{m}}$$

The resistance of an arbitrary conductor can be calculated from its specific electrical resistance  $\rho$ , its length  $L$  and its cross-sectional area  $A$  using:  $R = \rho \frac{L}{A}$ .

Table values (at 20°C):

Constantan:

$$\rho = 0,50 \frac{\Omega \cdot \text{mm}^2}{\text{m}}$$

Brass (37 % Zn, 63 % Cu):

$$\rho = 0,07 \frac{\Omega \cdot \text{mm}^2}{\text{m}}$$

## Apparatus

1 Apparatus for resistance measurements .....	550 57
2 Demo-Multimeter, passive .....	531 906
1 Power supply, 12 V, DC, 230 V .....	521 49
5 Connecting leads, 100 cm .....	500 444
2 Stand base, V-shape .....	300 02
2 Stand rods, 250 mm .....	300 41
2 Leybold multiclamp .....	301 01
2 Metal plate .....	from 686 50 ET5

## Carrying out the experiment

- Connect the constantan-wire ( $d = 0,5 \text{ mm}$ ).
- Set a voltage of  $0,5 \text{ V}$  on the power supply.
- Read current and voltage from the multimeter and write it into the table.
- Repeat the measurement with a brass-wire of identical cross-sectional area and length.
- Calculate resistances  $R$  from voltages  $U$  and currents  $I$  using ( $R = \frac{U}{I}$ ).

## Measuring example

Material	Voltage $U$ in V	Current $I$ in A	Resistance $R$ in $\Omega$
Constantan	0,50	0,20	2,50
Brass	0,50	1,40	0,36