

# Electronics with the Modular System


Basic Electronic Circuits  
Semiconductor diodes

## Characteristics of light-emitting diodes

### Objective of the experiment

To investigate the relationship between the voltage  $U$  and the current  $I$  for a light-emitting diode connected in forward direction.

### Setup

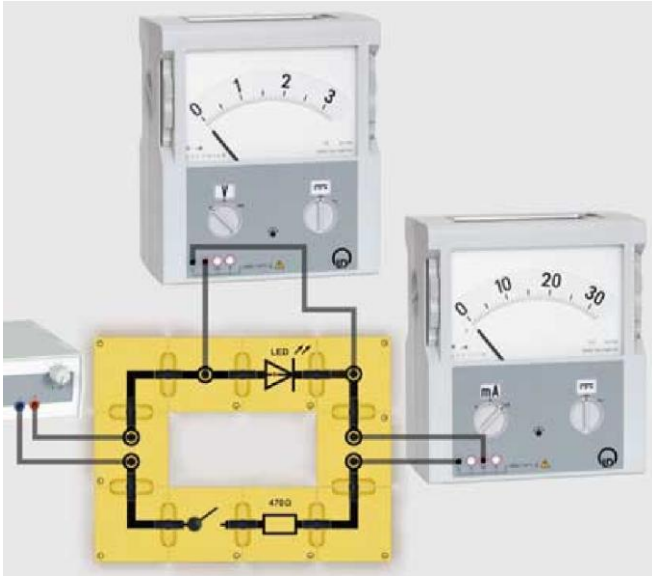

### Apparatus

1	539 037	Light-emitting diode, red, BST
1	539 038	Light-emitting diode, green, BST
1	539 010	Resistor 470 $\Omega$ , BST
1	539 025	Toggle switch, BST
1	539 002	Connector block BST, straight, 1 socket
2	539 003	Connector blocks BST, straight, 2 sockets
3	539 004	Connector blocks BST, 90° angle
1	539 006	Connector block BST, 90° angle with socket
10	539 000	Bridging plug, BST
2	531 905	Demo multimeter, passive
1	521 49	Power supply, 12 V DC, 230 V
6	500 644	Safety connection lead, 100 cm
1	301 300	Demonstration experiment frame
1	301 301	Adhesive magnetic board

### Carrying out the experiment

- Initially, set up the circuit with the red LED and close the toggle switch.
- Gradually increase the voltage  $U$  (see the table).
- For each voltage  $U$ , read the current  $I$  on the demo multimeter and observe the light-emitting diode.
- Replace the red LED with the green LED and repeat the experiment.


**Measuring example**

## Red LED

Voltage $U / V$	Current $I / \text{mA}$	LED lights up
0	0	no
1.0	0	no
1.4	0	no
1.5	1	yes (very dim)
1.55	3.5	yes
1.6	11.5	yes

## Green LED

Voltage $U / V$	Current $I / \text{mA}$	LED lights up
0	0	no
1.0	0	no
1.5	0	no
1.6	0	no
1.7	0	no
1.8	1	yes (very dim)
2.0	6.5	yes
2.2	16	yes

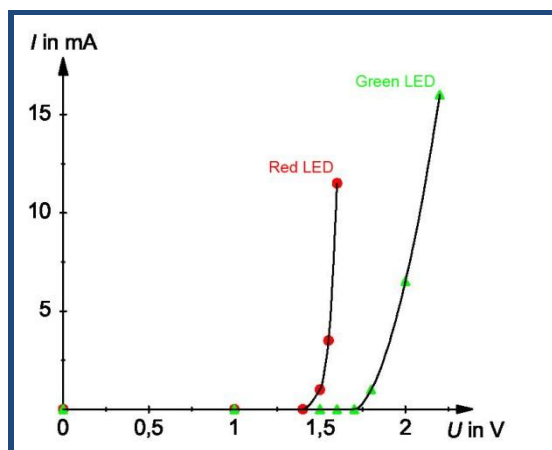**Evaluation**

Light-emitting diodes that emit different coloured lights differ in their characteristic voltages  $U_S$  (threshold voltage).

The threshold voltage  $U_S$  of a LED is reached when its light is clearly visible.

The threshold voltage  $U_S$  of the red LED is approx. 1.6 V.

The threshold voltage  $U_S$  of the green LED is approx. 2.0 V.